

Efficient Shop

Every article I've seen describing the wiring of a shop for both 120 volts and 240V uses separate cables for each voltage, which is a significant waste of time, effort and cable. Here I describe how a single cable can be used to provide both 120V and 240V service to a single two-gang wall box.

For many home woodworkers this wiring method is an easier, less expensive way to add 240V service to an existing 120V shop.

I describe only the connection scheme, and appropriate plugs and receptacles here. You should consult one of the many home wiring books carried at home centers for basic wiring instructions. I strongly suggest those inexperienced with electrical wiring practices (or those who aren't up-to-date on their local electrical codes) to contact a licensed electrician instead of attempting this on their own. Wiring requires a certain expertise.

The key to this system is the same technique employed for wiring an electric dryer or range, which uses a single cable to provide both 240V for the heating elements and 120V for the lights and motor: a three-wire-plus-ground cable. Using dedicated 240V circuits for heavy-current machines such as cabinet saws, planers, shapers, etc. is a very conservative approach for a one-man shop where only one heavy machine is in use at a time.

In my shop I employ a single 20-amp circuit to feed all the 120V and 240V machinery, plus a second 240V, 20-amp, two-conductor cable to feed the central dust collector. The use of a two-wire cable is permissible for 240V circuits if you color the white wire with a black or red magic marker at the connection points to indicate it is "hot." A second

by Bruce D. Wedlock

Bruce is a registered professional electrical engineer, an author of electrical engineering textbooks and a retired lecturer from the Massachusetts Institute of Technology. He practices woodworking in North Reading, Massachusetts. He can be reached at wedlock@alum.mit.edu.

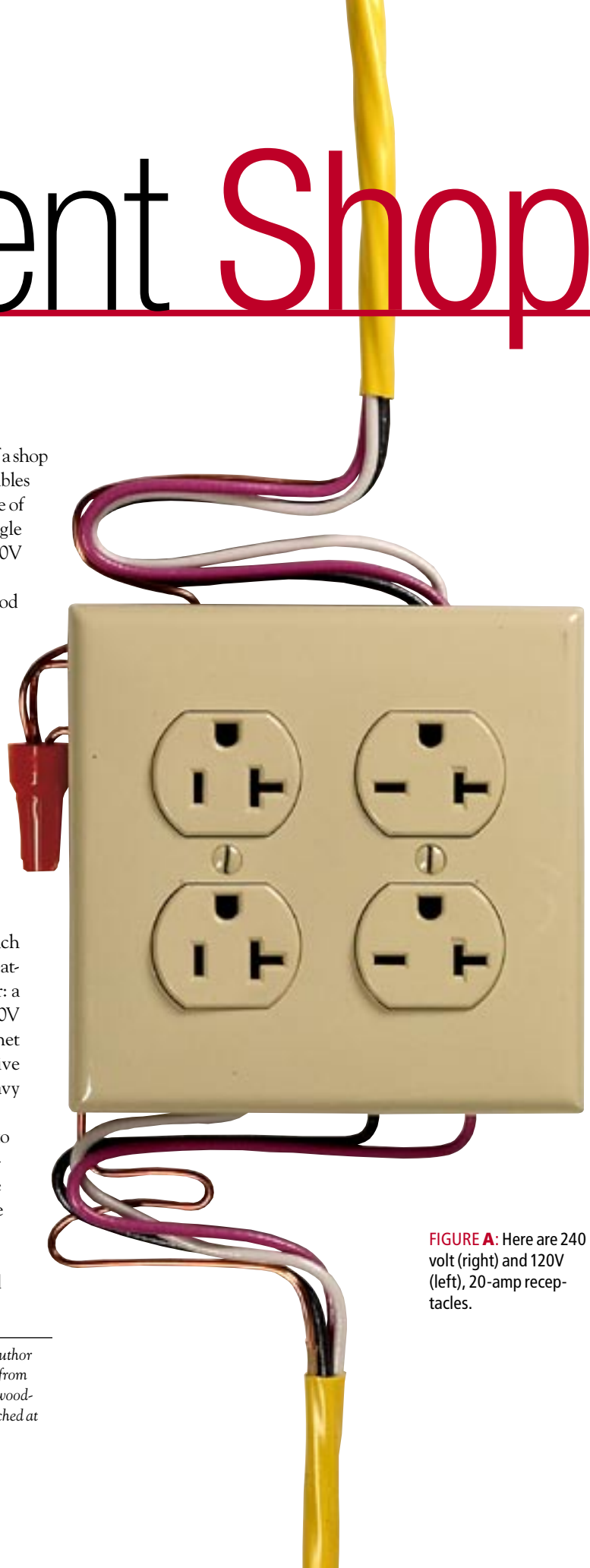


FIGURE A: Here are 240 volt (right) and 120V (left), 20-amp receptacles.

Wiring

A single cable provides
120-volt and 240V service.

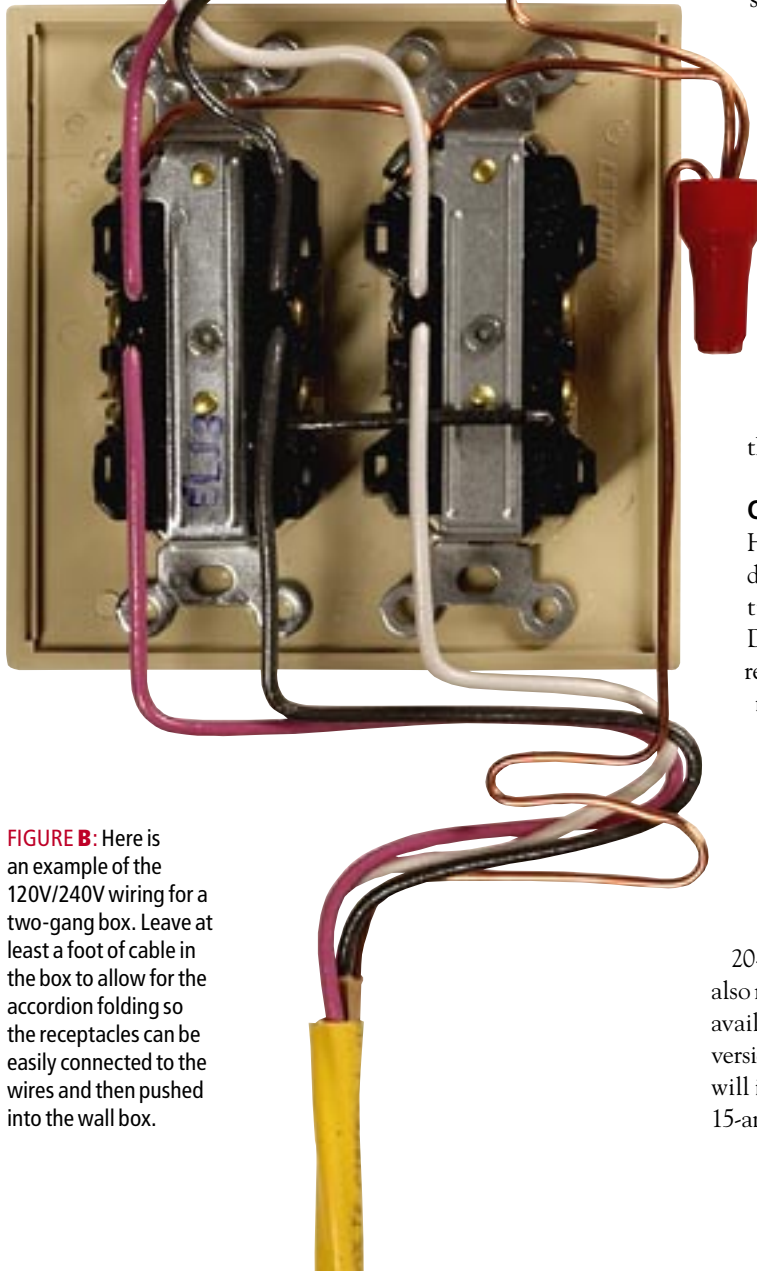


FIGURE B: Here is an example of the 120V/240V wiring for a two-gang box. Leave at least a foot of cable in the box to allow for the accordion folding so the receptacles can be easily connected to the wires and then pushed into the wall box.

three-wire cable provides dual 120V 20-amp circuits to round out the shop installation. These principles can be extended to multiple machine circuits, including automating the dust collector. (See “Easy Automatic Dust Control” on page XX.)

If the 120V receptacles are located in an unfinished space (garage or basement), the National Electric Code requires ground fault circuit interrupter (GFCI) protection. You should check with your town’s wiring inspector to see if your specific shop space requires GFCI receptacles. If it does, you will need a GFCI receptacle for each 120V outlet. If GFCI-protected 120V circuits are required, it may be more economical to run separate, conventional two-conductor circuits; one for 240V and one for 120V. The 120V circuit can then be protected with a single GFCI breaker and employ conventional receptacles. In that case you may want to use separate wall boxes for each voltage to reduce the wiring load in a box.

Component Selection

Heavy-duty commercial, “spec” or industrial-grade duplex receptacles should be used for shop applications; avoid residential or contractor grade units. Duplex receptacles rated for 20 amps at 125V are readily available. But 250V, 20-amp receptacles commonly found at home centers only have single outlets. Duplex 250V 20-amp receptacles are available, but you will probably have to go to an electrical supply house to obtain them.

Duplex receptacles provide twice as many outlet connections with no extra work so are well worth the effort to locate. Like clamps, you can’t have too many outlets. The Leviton No. 5462 is a duplex 250V, 20-amp receptacle available in brown or ivory. You will also need 250V male plugs for your machines. These are available at home centers, and come in 15- and 20-amp versions, which have different pin shapes, but either plug will insert into a 20-amp receptacle. I recommend the 15-amp plug for maximum flexibility. You might also want

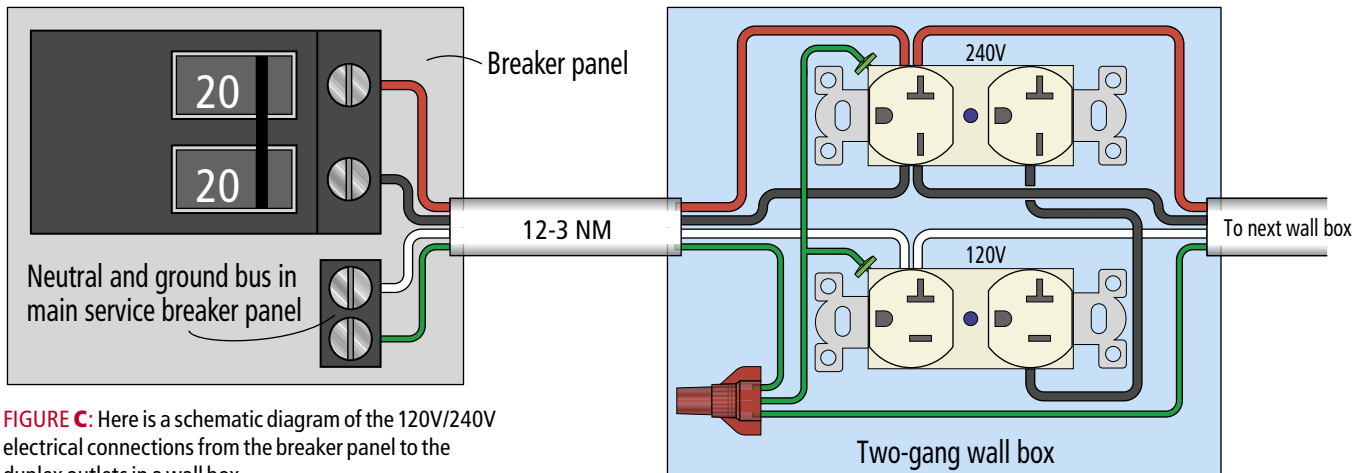


FIGURE C: Here is a schematic diagram of the 120V/240V electrical connections from the breaker panel to the duplex outlets in a wall box.

to purchase a matching 15-amp female connector and 14-gauge rubber covered cable to make a 240V extension cord. This cable should be two wires plus ground.

When buying receptacles, be sure to obtain units that can be backwired. It will greatly simplify your installation work. Backwiring means that you simply strip off a 1/2" length of insulation, insert the bare wire into a hole in the back of the receptacle and fasten it by tightening the corresponding screw. This is much easier than wrapping the bare wire around the screws, especially when making multiple connections in a wall box. Note: Early versions of backwired receptacles made the connection by spring pressure only. This type has been discontinued and is illegal for 20 amps in some locations. Be sure your backwired receptacles clamp the wire by tightening screws.

I find the two-gang PVC box most convenient for housing receptacles, but get the 2 3/4"-deep model. The shallow boxes won't hold the necessary wire and heavy-duty receptacles. These boxes are available for new work (when the studs are accessible) and old work (where sheetrock covers the studs). The latter are easily secured to the sheetrock surrounding the hole

cut for the box. If you're working with conduit, again get a deep box combination. A 2 1/4" box with a 1/2" cover will handle the receptacles and wiring.

Wiring a Wall Box For Machines

For 120V/240V shop applications I use three-wire 12 gauge nonmetallic (NM) sheathed cable, which is suitable for 20-amp circuits, and common-trip, two-pole, 20-amp circuit breakers. The cable actually contains four conductors, three insulated, colored red, black and white, plus a bare copper ground conductor. The white conductor is called the "neutral" while the bare copper wire is called the "ground."

All neutral and ground conductors are connected to the neutral bus bar in the main service breaker panel. The red and black conductors are connected to the circuit breaker terminals and carry the "live" voltages. A connection between the red and black conductors supplies 240V; a connection between the white and either the red or black conductor will provide 120V. So this single cable carries both voltages to the wall box receptacles.

In my shop, the wiring is all concealed behind walls, so NM cable is appropriate. If your shop has exposed wall wiring, use metal or plastic conduit on the exposed walls where the wiring is subject to physical damage.

The 120V/240V wall box connections are illustrated in Figure C, shown above. I prefer to make the through connections between the input and output cables in a backwired connection clamped by a single screw. The pigtail to feed the 120V receptacle's brass screw is backwired to the remaining screw on the black side of the 240V receptacle. Note: The white or neutral wire is only used for the 120V outlets and must always be connected to the silver screw. Photographs of the actual wiring is shown in Figure B, on page XX.

Ground connections are not backwired; they are made to the green, hexagonal screws, and must be wrapped clockwise around the screw head. The three ground

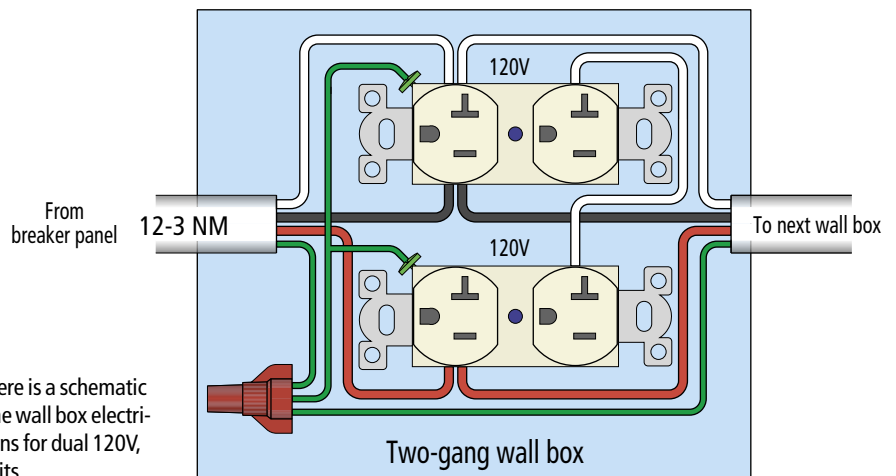


FIGURE D: Here is a schematic diagram of the wall box electrical connections for dual 120V, 20-amp circuits.

wires in the box are finally connected using a wire nut. When making these pigtail connections between the receptacles, you will find it convenient to temporarily attach the receptacles to the wall cover plate to hold them in the proper relationship while fastening these wires.

Additional 120V Circuits

It is good practice to have additional 120V circuits in your shop. Lights should never be on the same circuit as machines or they will dim when machines start. If you use appliances such as glue pots, hot plates, coffee pots, etc., which can be in continuous operation, they should also have a separate 120V circuit. These might be on when machines are also in use, leading to a tripped breaker if not on a separate circuit.

The good news is that if you add a 120V circuit, the use of 12-3 NM cable will permit two independent 20-amp circuits in one 4" wall box as illustrated in Figure D (at left). The connections at the breaker box are the same.

For safety, you must use common-trip, two-pole, 20-amp breakers to ensure all power to a wall box is off when the breaker is off. In the wall box, the neutral white wires are connected to the silver screws on the receptacles, and the black and red wires to the respective brass screws. The ground connections are the same. Again, this connection will not operate with GFCI protection unless each receptacle is GFCI. **PW**

Special thanks to Greg Hyland, who served as technical editor for this article. President of Cincinnati-based Cooper Electric, Hyland has been in the electrical trade for 35 years and holds Electrical Contractor licenses in Ohio and Kentucky, as well as Master Electrician licensed in five local jurisdictions.

EASY AUTOMATIC DUST CONTROL

When I installed my central dust collection system, I wanted automatic control. Turn on a machine and the collector comes on; turn off the machine and the collector goes off. No extra wiring, no klutzy strings and no "garage door opener" to misplace. The answer is a \$50 unit called the Automater (R.F. St. Louis 800-526-0602 or search online for "Automater"). It's the size of a deck of cards and neatly installs in a two-gang 2 1/4" metal handy box connected to your breaker panel with a nipple.

The Automater provides an adjustable turn-on delay to stagger the starting current surges of the machine and collector motors, plus a turn-off delay to clear the ducts. For a central dust collector installation you want the Model DC-2400. The schematic wiring diagram for the Automater is shown in Figure E (below). Note that the white wire from the 12-2 NM cable connected to the dust collector breaker has been colored black to indicate it is hot. A similar coloring is made in the connection box at the collector.

The Automater senses the current in the red machine conductor. When 3.5 amps is detected, it activates the dust collector by closing the T4 and T5 switch contacts. Hence, whenever a machine connected to the red conductor is turned on, the collector comes on after a few-second adjustable delay. When the machine is turned off, the collector stops after a similar delay. The commercial-grade SPST (single pole, single throw) switch wired to the T4 and T5 contacts permits the dust collector to be turned on manually without running a machine. This switch can be located at any convenient location in the shop. Connect to the Automater with 12-2 NM cable with white lead colored black.

The 120V/240V connection shown in Figure C (at left) used the black conductor to feed the 120V receptacle. However, if instead the red conductor were used to feed the 120V receptacle, then any tool plugged into that 120V outlet drawing a 3.5-amp current will also turn on the dust collector. So by feeding your 120V router table and chop saw outlets, for example, from the red conductor, they will also automatically control the dust collector.

The deciding factor whether or not a 120V receptacle connection controls the collector is whether it is fed from the red or black conductor. A single 120V duplex receptacle can also have it both ways. If the small tab between the two brass screws is broken off, then one 120V outlet can be connected to the black wire (no control) and the other connected to the red wire (control).

The single-cable connection scheme I've described can be expanded to larger shops by adding additional 20-amp breakers and woodworking machinery circuits. Automated dust collection will require a separate Automater for each breaker circuit with all the T4 and T5 switch terminals connected together, respectively. In that way whenever any machine is on, the dust collector will operate.

The Automater will also work with 240V three-phase machines. One only needs to feed one of the machine conductors through the T1 and T2 sensing contacts and connect either of the remaining machine conductors to the T3 terminal. When a machine is turned on, the T4 and T5 switch contacts will close. However, if the dust collector is also three-phase, an auxiliary relay will be needed to switch the collector's power. **-BW**

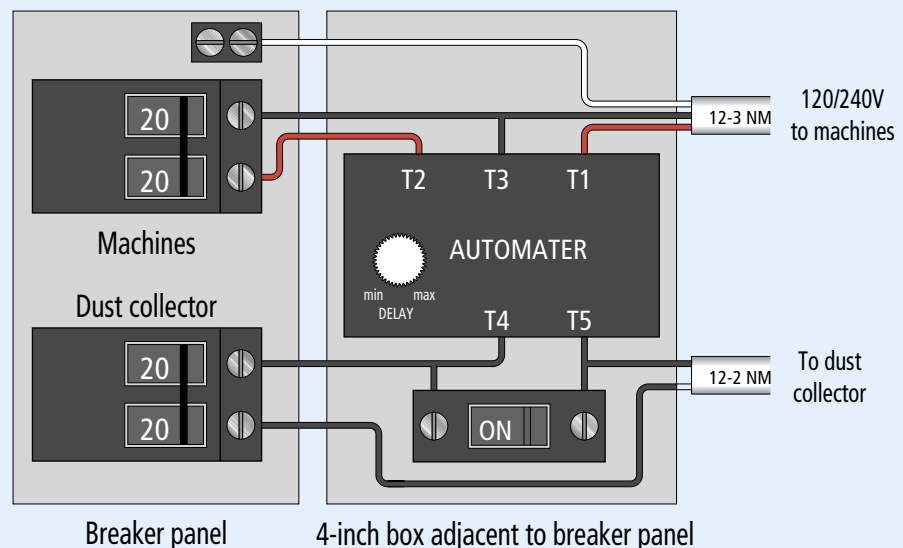


FIGURE E: Shown here is a schematic of connections for automatic dust collector control. Note the white 12-2 NM conductor has been colored black to identify both conductors as hot. The ground wiring is omitted for clarity.